

1. Parallel Adder:

Program

```
module adder4 ( carryin,x,y,sum,carryout);
input carryin;
input [3:0] x,y;
output [4:0] sum;
output carryout;
fulladd stage0 (carryin,x[0],y[0],sum[0],c1);
fulladd stage1 (c1,x[1],y[1],sum[1],c2);
fulladd stage2 (c2,x[2],y[2],sum[2],c3);
fulladd stage3 (c3,x[3],y[3],sum[3],carryout);
assign sum[4]=carryout;
endmodule
```

Testbench:

```
module adder4_t ;
reg [3:0] x,y;
reg carryin;
wire [4:0] sum;
wire carryout;
adder4 a1 (carryin,x,y,sum,carryout);
initial
begin
x = 4'b0000; y= 4'b0000;carryin = 1'b0;
#20 x =4'b1111; y = 4'b1010;
#40 x =4'b1011; y =4'b0110;
#40 x =4'b1111; y=4'b1111;
#50 $finish;
end
endmodule
```

```
module fulladd (cin,x,y,s,cout);
input cin,x,y;
output s,cout;
assign s = x^y^cin;
assign cout =( x & y) | (x & cin) |( y & cin);
endmodule
```

 


Fig.1 : Waveform of Parallel Adder

Synthesize the design using Constraints and analyse reports, critical path and Max Operating Frequency.

Step 1: Getting Started

Make sure you close out all the Incisive tool windows first.

Synthesis requires three files as follows, Liberty Files (.lib)

Verilog/VHDL Files (.v or .vhd or .vhd)

SDC (Synopsis Design Constraint) File (.sdc)

Step 2: Creating an SDC File

In your terminal type “gedit constraints_top.sdc” to create an SDC File if you do not have one.

The SDC File must contain the following commands

```
set_input_delay -max 0.8 [get_ports "A"]
set_input_delay -max 0.8 [get_ports "B"]
set_input_delay -max 0.8 [get_ports "C0"]
set_output_delay -max 0.8 [get_ports "S"]
set_output_delay -max 0.8 [get_ports "C4"]
```

Step 3 : Performing Synthesis

The Liberty files are present in the below path,

/home/install/FOUNDRY/digital/<Technology_Node_number>nm/dig/lib/

The Available technology nodes are 180nm ,90nm and 45nm.

In the terminal, initialise the tools with the following commands if a new terminal is being used.

```
csh source /home/install/cshrc
```

The tool used for Synthesis is “Genus”. Hence, type “**genus -gui**” to open the tool

 


Fig.1.2 : Schematic Capture of 4bit Adder

2. 4-bit Shift & Add Multiplier

```
module shift_add_multiplier(clk,reset,A,B,P);
    input clk,reset;
    input [3:0]A,B;    // Multiplicand and Multiplier
    output reg [7:0]P; // Product
    reg [7:0]multiplicand;
    reg [3:0]multiplier;
    reg [2:0]count;
    always @(posedge clk or posedge reset)
    begin
        if (reset)
            begin
                multiplicand <= 0;
                multiplier <= 0;
                P <= 0;
                count <= 0;
            end
        else
            begin
                if (count == 0)
                    begin
                        multiplicand <= {4'b0000, A}; // Extend A to 8 bits
                        multiplier <= B;
                        P <= 0;
                        count <= 4;
                    end
                else
                    begin
                        if (multiplier[0] == 1)
                            P <= P + multiplicand;

                        multiplicand <= multiplicand << 1;
                        multiplier <= multiplier >> 1;
                        count <= count - 1;
                    end
                end
            end
        end
    endmodule

module tb_multiplier;
    reg clk,reset;
    reg [3:0]A,B;
    wire [7:0]P;

    shift_add_multiplier uut(clk,reset,A,B,P);
    initial
    clk = 0;
    always #5 clk = ~clk;
    initial
    begin
        reset = 1;
        #10 reset = 0;
        A = 4'b0101; // 5
        B = 4'b0011; // 3
    #50
        A = 4'b1011; // 11
        B = 4'b0111; // 7
    end
endmodule
```

```
#50 $finish;  
end  
endmodule
```

 


Fig:2. Waveform of shift & add multiplier

3. a. 32-bit ALU using case statement

```

module alu_32bit_case(y,a,b,f);
input [31:0]a;
input [31:0]b;
input [2:0]f;
output reg [31:0]y;
always@(*)
begin
case(f)
3'b000:y=a&b; //AND Operation
3'b001:y=a|b; //OR Operation
3'b010:y=~(a&b); //NAND Operation
3'b011:y=~(a|b); //NOR Operation
3'b100:y=a+b; //Addition
3'b101:y=a-b; //Subtraction
3'b110:y=a*b; //Multiply
default:y=32'bx;
endcase
end
endmodule
//Test Bench//
module alu_32bit_tb_case;
reg [31:0]a;
reg [31:0]b;
reg [2:0]f;
wire [31:0]y;
alu_32bit_case test2 (y,a,b,f);
initial
begin
a=32'h00000000;
b=32'hFFFFFFFF;
#10 f=3'b000;
#10 f=3'b001;
#10 f=3'b010;
#10 f=3'b100;
#10 f=3'b101;
#10 f=3'b110;
#10 f=3'b111;
#50 $finish;
end
endmodule

```

 


Fig.3a.: Waveform of ALU

3. b. 32-bit ALU using if else statement

```

module alu_32bit_if(y,a,b,f);
input [31:0]a;
input [31:0]b;
input [2:0]f;
output reg [31:0]y;
always@(*)
begin
if(f==3'b000)
y=a&b; //AND Operation
else if (f==3'b001)
y=a|b; //OR Operation
else if (f==3'b010)
y=a+b; //Addition
else if (f==3'b011)
y=a-b; //Subtraction
else if (f==3'b100)
y=a*b; //Multiply
else
y=32'bx;
end
endmodule

//Test bench //
module alu_32bit_tb_if;
reg [31:0]a;
reg [31:0]b;
reg [2:0]f;
wire [31:0]y;
alu_32bit_if test(y,a,b,f);
initial
begin
a=32'h00000000;
b=32'hFFFFFFFF;
#10 f=3'b000;
#10 f=3'b001;
#10 f=3'b010;
#10 f=3'b100;
#10 f=3'b101;
#50 $finish;
end
endmodule

```

 


Fig.3b.: Waveform of ALU

4.Verilog code for flip flops

D flip flop

```
module dff1(q,qb,clk,rst,din);
input clk,rst,din;
output reg q;
output qb;
always @(posedge clk or posedge rst)
begin
if(rst)
q<=1'b0;
else
q<=din;
end
assign qb= ~q;
endmodule
//test bench//
module dff_t;
reg clk,din,rst;
wire q,qb;
dff1 U1(q,qb,clk,rst,din);
initial
clk=1'b0;
always
#10 clk=~clk;
initial
begin
din=1'b0;
rst=1'b1;
#20 rst=1'b0'
#10 din=1'b1;
#15 rst=1'b1;
#18 din=1'b0
#1 din=1'b1;
#20 din=1'b0;
#10 $finish;
end
endmodule
```

 


Fig.4a.: Waveform of D-Flipflop

JK flip flop

```
module jk_ff(q,qbar,clk,rst,j,k);
input clk,rst,j,k;
output q,qbar;
reg q,tq;
always@(posedge clk or negedge rst)
begin
if(!rst)
begin
q<=1'b0;
tq<=1'b0;
end
else
begin
if(j==1'b1 && k==1'b0)
q<=j;
else if(j==1'b0 && k==1'b1)
q<=1'b0;
else if(j==1'b1 && k==1'b1);
begin
tq<=~tq;
q<=tq;
end
end
end
assign qbar=~q;
endmodule

//Testbench//
module jk_ff_test;
reg clk,rst,j,k;
wire q,qbar;
jk_ff inst(q,qbar,clk,rst,j,k);
initial
clk=1'b0;
always
#10 clk=~clk;
initial
begin
j=1'b0;k=1'b0;rst=1'b0;
#30 rst=1'b1;
#60 k=1'b1;
#29 j=1'b1;
#15 k=1'b1;
#20 j=1'b0;
#40 j=1'b1;
#25 k=1'b0;
#5 j=1'b0;
#50 rst=1'b0;
#10 $finish;
end
endmodule
```

 


Fig.4b.: Waveform of JK-Flipflop

SR flip flop

```

module SR_ff(q,qbar,s,r,clk,rst);
output q,qbar;
input clk,s,r,rst;
reg tq;
always @(posedge clk or rst)
begin
if(s==1'b0&&r==1'b0)
tq<=tq;
else if(s==1'b0&&r==1'b1)
tq<=1'b0;
else if(s==1'b1&&r==1'b0)
tq<=1'b1;
else if(s==1'b1&&r==1'b1)
tq<=1'bx;
end
assign q=tq;
assign qbar=~tq;
endmodule
//Test bench//
module SR_ff_t;
reg clk,s,r,rst;
wire q,qbar;
SR_ff ff1(q,qbar,s,r,clk);
initial
clk=1'b0;
always
#10 clk=~clk;
initial
begin
s=1'b0;r=1'b0;rst=1'b0;
#30 s=1'b1;
#29 s=1'b0;

```

```

#1 r=1'b1;rst=1'b1;
#30 s=1'b1;
#15 rst=1'b0;
#30 r=1'b0;
#20 s=1'b0;
#19 s=1'b1;
#200 s=1'b1;r=1'b1;
#50 s=1'b0;r=1'b0;
#50 s=1'b1;r=1'b0;
#10 $finish;
end
endmodule

```

 


Fig.4c.: Waveform of SR-Flipflop

5a. Verilog code for synchronous counter

```
module counter(clk,rst,m,count);
input clk,rst,m;
output reg [3:0]count;
always @(posedge clk or negedge rst)
begin
if(!rst)
count=0;
else if(m)
count=count+1;
else
count=count-1;
end
endmodule
//test bench//
module counter_test;
reg clk,rst,m;
wire [3:0]count;
counter counter1(clk,rst,m,count);
initial
clk=0;
always
#5 clk= ~clk;
initial
begin
rst=0; m=0; // Condition for Up-Count
#25
rst=1;
m=1;
#200 m=0; // Condition for Down-Count
#25 rst=1;
#200 m=1;
#140 m=0;
#250 $finish; // Finishing Simulation at t=140ns
end
endmodule
```

 


Fig: waveform of synchronous counter

5.b Asynchronous counter

```
module ripple_counter(clock,toggle,reset,count);
input clock,toggle,reset;
output [3:0]count;
reg [3:0]count;
wire c0,c1,c2;
assign c0 = count[0],c1 = count[1],c2 = count[2];

always @ (posedge reset or posedge clock)
    if (reset == 1'b1) count[0] <= 1'b0;
    else if (toggle == 1'b1) count[0] <= ~count[0];

always @ (posedge reset or negedge c0)
    if (reset == 1'b1) count[1] <= 1'b0;
    else if (toggle == 1'b1) count[1] <= ~count[1];

always @ (posedge reset or negedge c1)
    if (reset == 1'b1) count[2] <= 1'b0;
    else if (toggle == 1'b1) count[2] <= ~count[2];

always @ (posedge reset or negedge c2)
    if (reset == 1'b1) count[3] <= 1'b0;
    else if (toggle == 1'b1) count[3] <= ~count[3];
endmodule

//Test bench structure

module ripple_counter_t ;
reg clock,toggle,reset;
wire [3:0] count ;
ripple_counter r1 (clock,toggle,reset,count);
initial
    clock = 1'b0;
always
    #5 clock = ~clock;
initial
begin
    reset = 1'b0; toggle = 1'b0;
    #10 reset = 1'b1; toggle = 1'b1;
    #10 reset = 1'b0;
    #190 reset = 1'b1;
    #20 reset = 1'b0;
    #100 reset = 1'b1;
    #40 reset = 1'b0;
    #25 $finish;
end
endmodule
```

 


Fig: waveform of asynchronous counter

6. Inverter

 


Fig. 6;1: Schematic of Inverter $W_n=W_p$

 


Fig. 6;2: Schematic of Inverter $W_p=W_n/2$

 


Fig. 6;3: Schematic of Inverter $W_p=2W_n$

 


Fig. 6;4: Symbol of Inverter

 


Fig. 6;5: Test generation of Inverter

 


Fig. 6;6: Simulated waveforms of Inverter

Table –1 : Values of t_{pHL} , t_{pLH} and t_{pD} for different geometries

Width Settings	MOSFET	Width	t_{pLH}	t_{pHL}	t_{pD}
$W_p = W_n$	PMOS				
	NMOS				
$W_n = 2W_p$	PMOS				
	NMOS				
$W_n = W_p/2$	PMOS				
	NMOS				

 


Fig. 6.7: Layout of Inverter

 


Fig.6.8: Result of DRC Check if the layout is DRC clean

 


Fig.6.9: "LVS Debug" window

 


Fig.6.10: Extracted View

Table – 2: Values of tp_{HL} , tp_{LH} and tp_D for CMOS Inverter with $WPWN=4/2$

MOSFET	Length	Width	tp_{LH}	tp_{HL}	tp_D
PMOS	180n				
NMOS	180n				

7. Two Input CMOS NOR Gate

 


Fig.7.1: Schematic of NOR Gate

 


Fig.7.2: Symbol of NOR Gate

 


Fig.7.3: Test generation of NOR Gate

 


Fig.7.4: Waveforms of NOR Gate

Delay Elements for 2 – input CMOS NOR Gate (Prelayout Simulation)

MOSFET	Length	Width	tpLH	tpHL	tpd
PMOS	180n				
NMOS	180n				

 


Fig.7.5: Layout of NOR Gate

Delay Elements for 2 – input CMOS NOR Gate (Post layout Simulation)

MOSFET	Length	Width	tpLH	tpHL	tpd
PMOS	180n				
NMOS	180n				

8. Construct the schematic using Boolean Expression using CMOS-Logic $Y = \overline{(B+CD+E)}$

 


Fig.8.1: Schematic of Boolean expression using CMOS-logic

 


Fig.8.2: Symbol of Boolean expression using CMOS-logic

 


Fig.8.3: Test generation of Boolean expression using CMOS-logic



Fig.8.4: Output Waveforms of Boolean expression using CMOS-logic.

9. Common Source Amplifier With PMOS Current Mirror Load

 


Fig.9.1: Schematic of Common Source Amplifier with PMOS Current Mirror Load

 


Fig.9.2: Symbol of Common Source Amplifier with PMOS Current Mirror Load

 


Fig.9.3: Test generation of Common Source Amplifier with PMOS Current Mirror Load

 


Fig.9.4: Output Waveforms of Common Source Amplifier with PMOS Current Mirror Load

 


Fig.9.5: Output Waveforms - AC analysis of Common Source Amplifier with PMOS Current Mirror Load

 


Fig.9.6: Output Waveforms – Gain and Phase plots of Common Source Amplifier

 


Fig.9.7: Layout of Common Source Amplifier with PMOS Current Mirror Load

09. Two Stage Operational Amplifier

 


Fig.10.1: Schematic of 2 – Stage Operational Amplifier

 


Fig.10.2: Symbol for 2 – Stage Operational Amplifier

 


Fig.10.3: Test Schematic for 2 – Stage Operational Amplifier

 


Fig.10.4: Output Waveforms

 


Fig.10.5: DC Open Loop Gain

 


Fig.10.6: Unity Gain Bandwidth

 


Fig.10.7: Layout for 2 – Stage Operational Amplifier

Demonstration Experiments:

11. UART- Universal Asynchronous Synchronous Receiver

uart_ROUTED_NETLIST.v

```
`timescale 1 ns / 1 ps
module uart (
    reset          ,
    txclk          ,
    ld_tx_data     ,
    tx_data        ,
    tx_enable      ,
    tx_out         ,
    tx_empty       ,
    rxclk          ,
    uld_rx_data    ,
    rx_data        ,
    rx_enable      ,
    rx_in          ,
    rx_empty       ,
);
// Port declarations
input      reset          ;
input      txclk          ;
input      ld_tx_data     ;
input [7:0] tx_data       ;
input      tx_enable      ;
output     tx_out         ;
output     tx_empty       ;
input      rxclk          ;
input      uld_rx_data    ;
output [7:0] rx_data       ;
input      rx_enable      ;
input      rx_in          ;
output     rx_empty       ;

// Internal Variables
reg [7:0] tx_reg          ;
reg      tx_empty        ;
reg      tx_over_run     ;
reg [3:0] tx_cnt         ;
reg      tx_out          ;
reg [7:0] rx_reg          ;
reg [7:0] rx_data         ;
reg [3:0] rx_sample_cnt   ;
reg [3:0] rx_cnt          ;
reg      rx_frame_err     ;
reg      rx_over_run      ;
reg      rx_empty        ;
reg      rx_d1            ;
reg      rx_d2            ;
reg      rx_busy          ;
```

// UART_RX_End

```

        // Check if last rx data was not unloaded,
        rx_over_run <= (rx_empty) ? 0 : 1;
    end
end
end
end
end
end
if ( ! rx_enable) begin
    rx_busy <= 0;
end
end
// UART TX Logic
always @ (posedge txclk or posedge reset)
if (reset) begin
    tx_reg        <= 0;
    tx_empty      <= 1;
    tx_over_run   <= 0;
    tx_out        <= 1;
    tx_cnt        <= 0;
end else begin
    if (ld_tx_data) begin
        if ( ! tx_empty) begin
            tx_over_run <= 0;
        end else begin
            tx_reg <= tx_data;
            tx_empty <= 0;
        end
    end
    if (tx_enable && ! tx_empty) begin
        tx_cnt <= tx_cnt + 1;
        if (tx_cnt == 0) begin
            tx_out <= 0;
        end
        if (tx_cnt > 0 && tx_cnt < 9) begin
            tx_out <= tx_reg[tx_cnt - 1];
        end
        if (tx_cnt == 9) begin
            tx_out <= 1;
            tx_cnt <= 0;
            tx_empty <= 1;
        end
    end
    if ( ! tx_enable) begin
        tx_cnt <= 0;
    end
end
end
endmodule

```

```

// UART RX Logic
always @ (posedge rxclk or posedge reset)
if (reset) begin
    rx_reg        <= 0;
    rx_data       <= 0;
    rx_sample_cnt <= 0;
    rx_cnt        <= 0;
    rx_frame_err  <= 0;
    rx_over_run   <= 0;
    rx_empty      <= 1;
    rx_d1         <= 1;
    rx_d2         <= 1;
    rx_busy       <= 0;
end else begin
// Synchronize the asynch signal
    rx_d1 <= rx_in;
    rx_d2 <= rx_d1;
// Uload the rx data
    if (uld_rx_data) begin
        rx_data <= rx_reg;
        rx_empty <= 1;
    end
// Receive data only when rx is enabled
    if (rx_enable) begin
        // Check if just received start of frame
        if ( ! rx_busy && ! rx_d2) begin
            rx_busy      <= 1;
            rx_sample_cnt <= 1;
            rx_cnt       <= 0;
        end
        // Start of frame detected, Proceed with rest of data
        if (rx_busy) begin
            rx_sample_cnt <= rx_sample_cnt + 1;
            // Logic to sample at middle of data
            if (rx_sample_cnt == 7) begin
                if ((rx_d2 == 1) && (rx_cnt == 0)) begin
                    rx_busy <= 0;
                end else begin
                    rx_cnt <= rx_cnt + 1;
                    // Start storing the rx data
                    if (rx_cnt > 0 && rx_cnt < 9) begin
                        rx_reg[rx_cnt - 1] <= rx_d2;
                    end
                    if (rx_cnt == 9) begin
                        rx_busy <= 0;
                    end
                end
            end
        end
    end
end

```

```

//generate rxclk and txclk so that txclk is 16 times slower than rxclk
reg [3:0] counter;
initial begin
    rxclk=0;
    txclk=0;
    counter=0;
end
always @(posedge clk) begin
    counter<=counter+1;
    if (counter == 15) txclk <= ~txclk;
    rxclk<= ~rxclk;
end

//setup loopback
always @ (tx_out) rx_in=tx_out;

    initial begin
        // Initialize Inputs
        reset = 1;
        ld_tx_data = 0;
        tx_data = 0;
        tx_enable = 1;
        uld_rx_data = 0;
        rx_enable = 1;
//        rx_in = 1;

        // Wait 100 ns for global reset to finish
        #500;
        reset = 0;

        // Send data using tx portion of UART and wait until data is recieved
        tx_data=8'b0111_1111;
        #500;
        wait (tx_empty==1); //make sure data can be sent
        ld_tx_data = 1; //load data to send
        wait (tx_empty==0); //wait until data loaded for send
        $display("Data loaded for send");
        ld_tx_data = 0;
        wait (tx_empty==1); //wait for flag of data to finish sending
        $display("Data sent");
        wait (rx_empty==0); //wait for
        $display("RX Byte Ready");
        uld_rx_data = 1;
        wait (rx_empty==1);
        $display("RX Byte Unloaded: %b",rx_data);
        #100;

        $finish;
    end
endmodule

```

 


Fig.10.7: Simulation Waveform of UART

12. SRAM: Implementation of 6T-SRAM

 


Fig.12.1: Schematic of SRAM

 


Fig.12.2: Symbol of SRAM



Fig.12.3: Output of SRAM read

 


Fig.12.4: Layout of SRAM Cell.